

Exercises for Experimental Physics 3 – IPSP

Prof. Dr. J. Käs, Dr. M. Zink

Exercise Sheet 4 (WS 2010/11)

Date of Issue to Students: Nov. 4th 2010

Date of Submission: Nov. 11th 2010

Submission Place: Marked mailbox next to room 302 (Linnestr. 5)

Submission Time: 11:00 a.m. at the submission day noted above

Please note: Write your name and matriculation number on EACH sheet of paper. Only submit the calculations and results for exercise 1-3, exercise 4 will be discussed during the instruction classes.

Exercises:

1. A coil that has a resistance of 80.0Ω has an impedance of 200Ω when driven at a frequency of 1.00 kHz . What is the inductance of the coil? (3 Points)
2. A series RLC circuit that has an inductance of 10 mH , a capacitance of $2.0 \mu\text{F}$, and a resistance of 5.0Ω is driven by an ideal ac voltage source that has a peak voltage of 100 V . Find (a) the resonant frequency and (b) the root-mean-square current at resonance. When the frequency is 8000 rad/s , find (c) the capacitive and inductive reactances, (d) the impedance, (e) the root-mean-square current, and (f) the phase angle. (7 Points)
3. An ideal 0.25-H inductor and a capacitor are connected in series with an ideal 60-Hz generator. A digital voltmeter is used to measure the rms voltages across the inductor and capacitor independently. The voltmeter reading across the capacitor is 75 V and that across the inductor is 50 V . (a) Find the capacitance and the rms current in the circuit. (b) What is the rms voltage across the series combination of the capacitor and the inductor? (5 Points)
4. Figure 1 shows an inductor in series with a parallel plate capacitor. The capacitor has a width w of 20 cm and a gap of 2.0 mm . A dielectric that has a dielectric constant of 4.8 can be slid in and out of the gap. The inductor has an inductance of 2.0 mH . When half the dielectric is between the capacitor plates (when $x = \frac{1}{2}w$), the resonant frequency of this combination is 90 MHz . (a) What is the capacitance of the capacitor without the dielectric? (b) Find the resonance frequency as a function of x for $0 \leq x \leq w$.

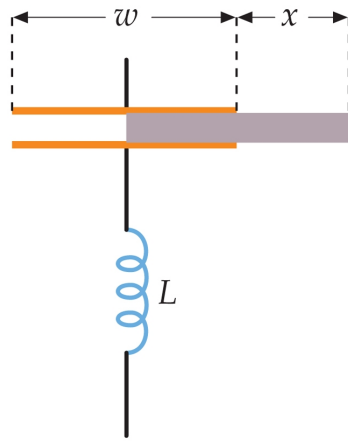


Figure 1: Exercise 4